

3. Construct a logic diagram for the following expression.

NOT A OR (A AND B)

[3]